

ALU harder
than
Sat Contr

ENGR 210 / CSCI B441
"Digital Design"

Lag
Test

Sequential Logic

FSMs

Andrew Lukefahr

Announcements

- P7 Saturating Counter is out
- P8 – Elevator Controller is out
 - This one is hard.

← due Friday ☹️

← start early

Always specify
defaults for
always_comb!


Inferred Latches are bad...

```
WARNING: [Synth 8-327] inferring latch for  
variable 'count_reg'  
[/home/autograder/working_dir/src/saturating_cou  
nter.sv:XX]
```


BLOCKING (=) FOR
always_comb



NON-BLOCKING (<=) for
always_ff

D Latch versus D Flip-Flop

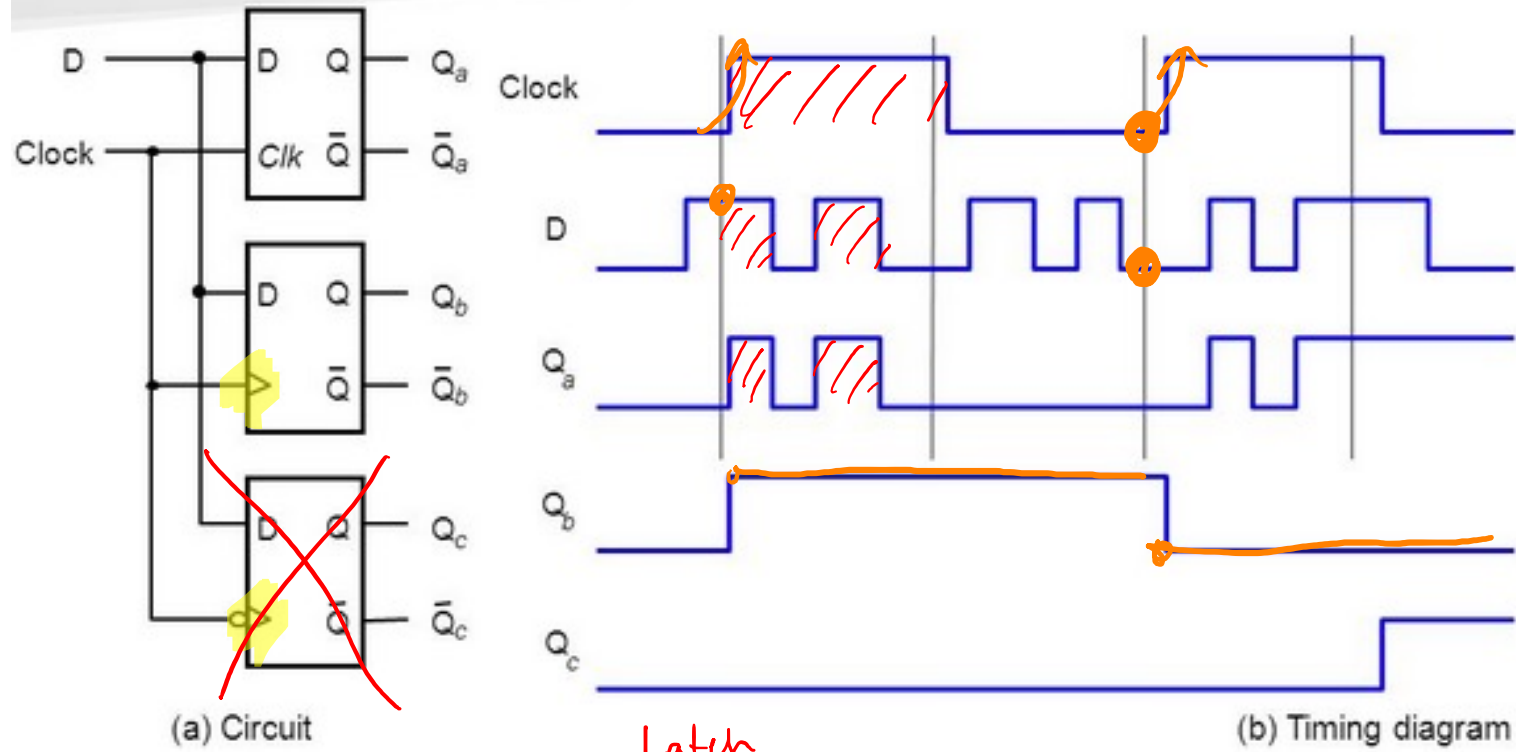

Comparison of level-sensitive and edge-triggered devices

Glitches on D-Latches

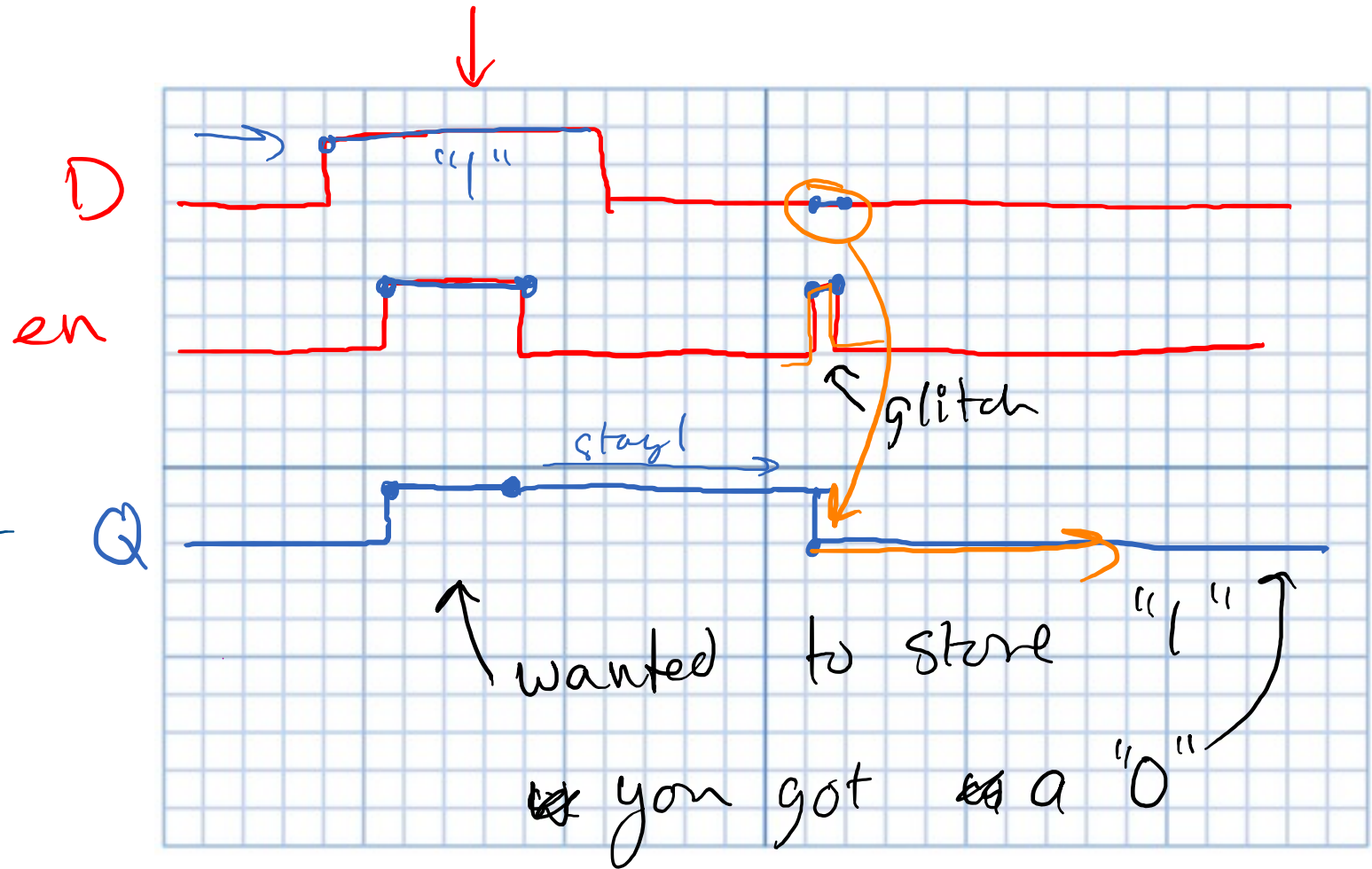 

Flip-Flop in Verilog

```
module d_ff (
    input      d,    //data
    input      clk,  //clock
    output logic q    //output register
);

    always_ff @( posedge clk )
    begin
        q <= d; //non-blocking assign
    end

endmodule
```

Shift-Register in Verilog

```

module shift_register (
    input clk, rst, D,
    output [3:0] Q );

    logic [3:0] dff;
    logic [3:0] next_dff;

    always_ff(@posedge clk) begin
        if (rst) dff <= 4'h0;
        else     dff <= next_dff;
    end



    always_comb
        next_dff = { dff[2:0], D};

    assign Q = dff;


endmodule

```

logic [3:0] a;
logic [0:3] b;

 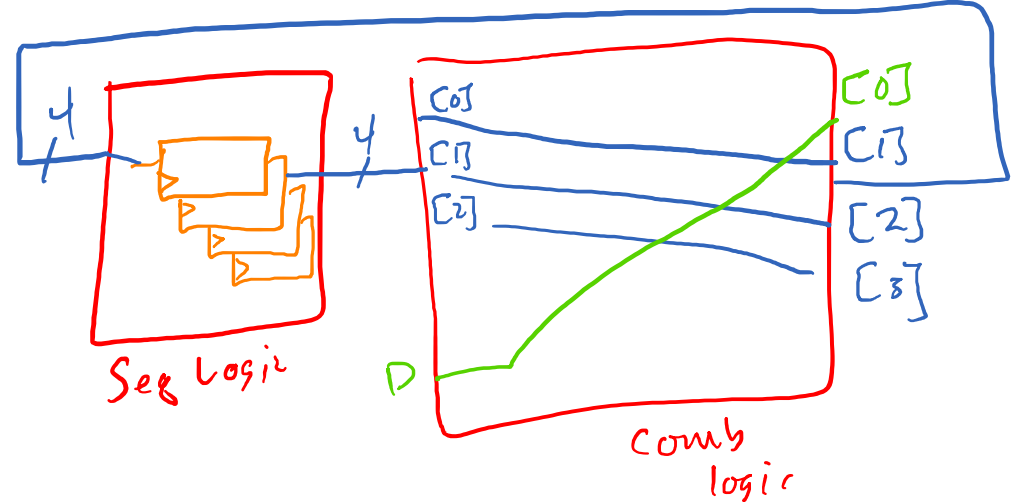


assign b = a;

 

Shift-Register in Verilog
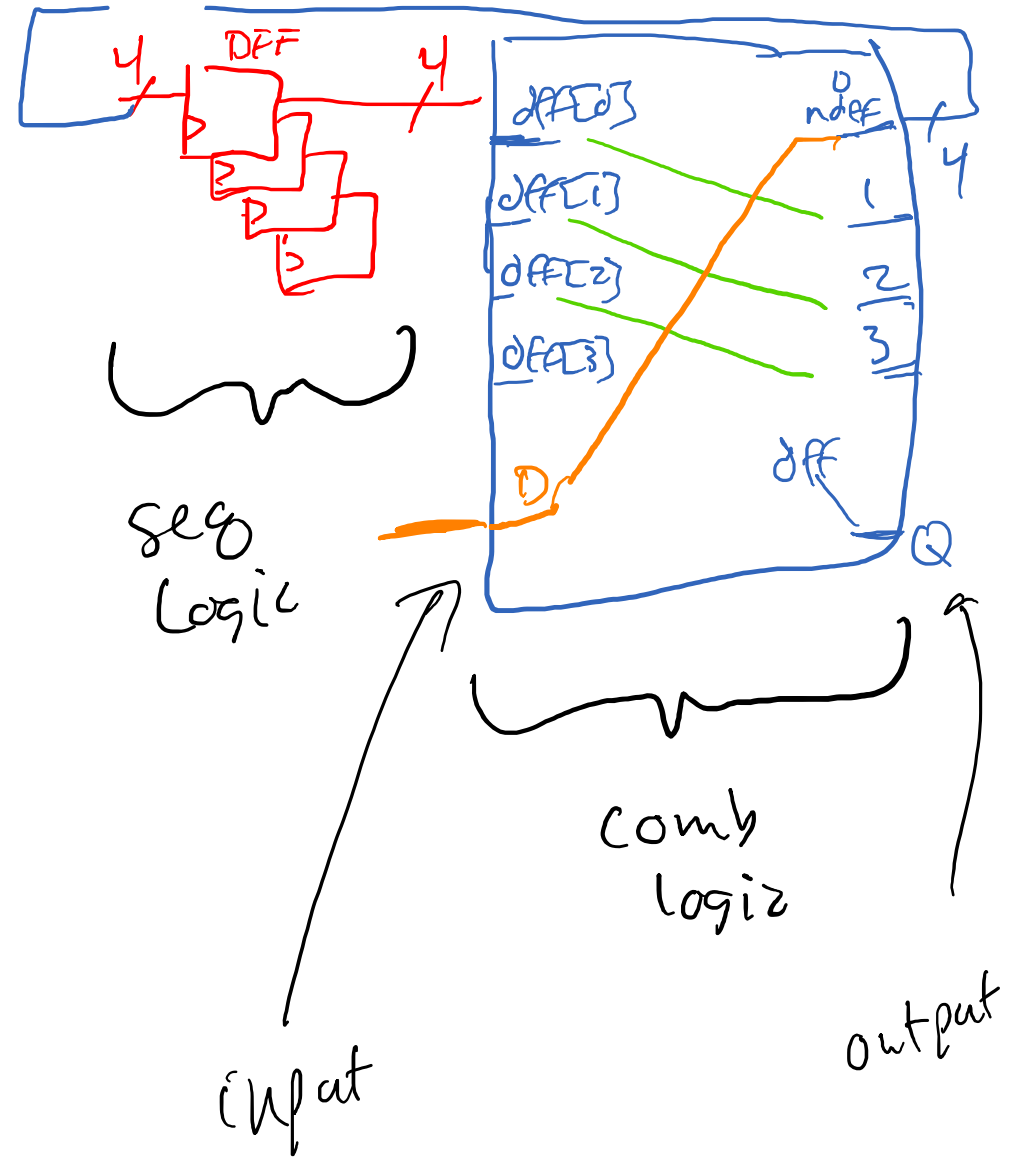
```
module shift_register (  
    input clk, rst, D,  
    output [3:0] Q );  
  
    logic [3:0] dff;  
    logic [3:0] next_dff;  
  
    always_ff(@posedge clk) begin  
        if (rst) dff <= 4'h0;  
        else     dff <= next_dff;  
    end  
  
    always_comb  
        next_dff = { dff[2:0], D};  
  
    assign Q = dff;  
  
endmodule
```



What does this module do?

```
module mystery(
    input          clk,      //clock
    input          rst,      //reset
    output logic   out       //output
);
    logic [3:0] Q;
    logic [3:0] sum;

    always_ff @( posedge clk ) // <- sequential logic
    begin
        if (rst) Q <= 4'h0;
        else     Q <= sum;     //non-blocking
    end

    always_comb begin // <- combinational logic
        sum = Q + 4'h1; //blocking
        out = sum[3];
    end

endmodule
```

What does this module do?



0 = 0000
 1 = 0001
 2 = 0010
 3 = 0011

```

module counter(
    input          clk,      //clock
    input          rst,      //reset
    output logic   out       //output
);
    logic [3:0] Q;
    logic [3:0] sum;

    always_ff @( posedge clk ) // <- sequential logic
    begin
        if (rst) Q <= 4'h0;
        else    Q <= sum;      //non-blocking
    end


    always_comb begin // <- combinational logic
        sum = Q + 4'h1; //blocking
        out = sum[3];
    end
endmodule

```


Sum = 7
0111

Sum = 8
1000


Sum = 15

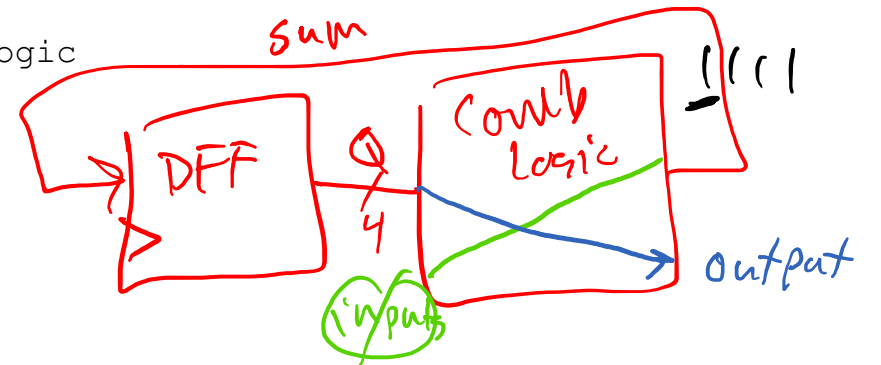

 Sequential Logic uses both Flip-Flops and Combinational Logic



Inputs can affect output or state

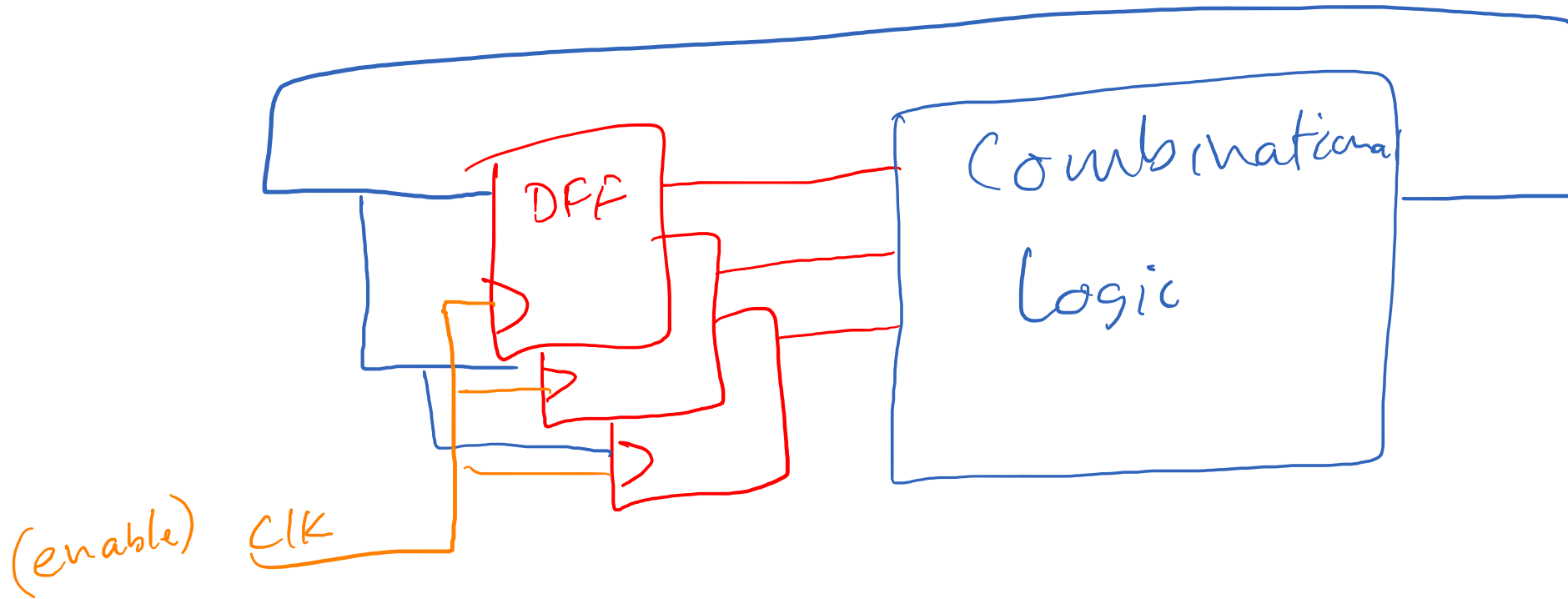


What's wrong here?

```
logic [1:0] count;

always_comb begin
    count = count; //default

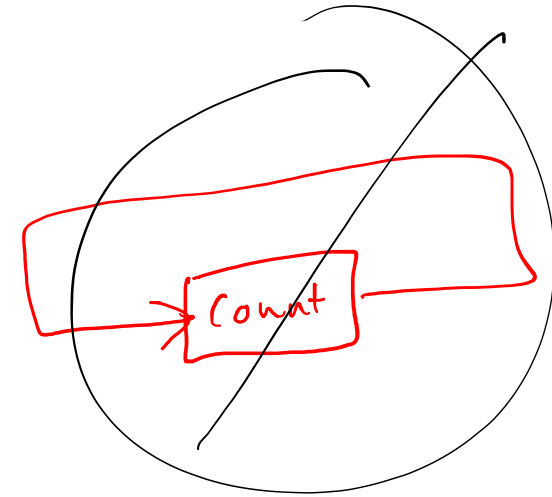    if (foo) begin
        count = count + 1;
    end else if (bar) begin
        count = count - 1;
    end
end
```




What's wrong here?

```
logic [1:0] count;

always_comb begin
    count = count; //not a default

    if (foo) begin
        count = count + 1; //self reference
    end else if (bar) begin
        count = count - 1; //self reference
    end
end

end
```

 


Count needs to be stateful.

```
logic [1:0] count, nextCount;

always_ff @(posedge clk) begin
    if (rst) count <= 2'h0;
    else     count <= nextCount;
end

always_comb begin
    nextCount = count; //default

     if (foo) begin
        nextCount = count + 1;
    end else if (bar) begin
        nextCount = count - 1;
    end
end
```




Finite State Machines (FSMs)

Finite State Machines (FSMs)


- A **finite-state machine (FSM)** or **finite-state automaton (FSA**, plural: *automata*), **finite automaton**, or simply a **state machine**, is a mathematical [model of computation](#).
- It is an [abstract machine](#) that can be in exactly one of a finite number of [states](#) at any given time.
- The FSM can change from one state to another in response to some [inputs](#); the change from one state to another is called a *transition*.^[1]
[wiki]

States, Transitions, and Guards

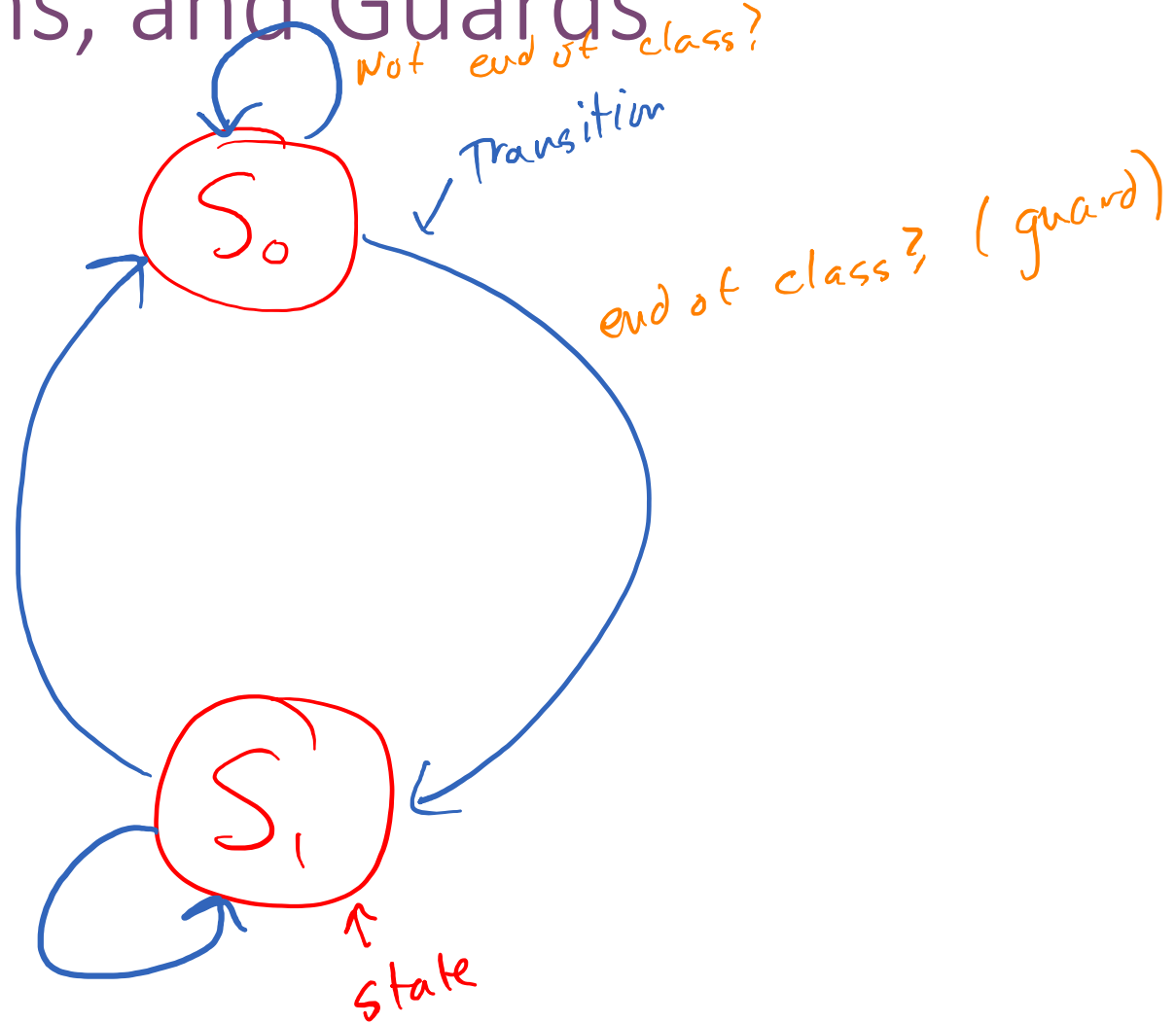

FSM: Traffic Signal Controller

 - A controller for traffic at the intersection of a main highway and a country road.



- The main highway gets priority because it has more cars
 - The main highway signal remains **green** by default.

Traffic signal controller

Tractors

- ~~Cars~~ occasionally arrive from the country road. The traffic signal for the country road must turn **green** only long enough to let the cars on the country road go.
- When no cars are waiting on the country road, the country road traffic signal turns **yellow** then **red** and the traffic signal on the main highway turns **green** again.

There is a sensor to detect cars waiting on the country road. The sensor sends a signal X as input to the controller:



$X = 1$, if there are cars on the country road

$X = 0$, otherwise



$$\overline{X} = !X = \text{NOT } X$$

What are the 'States'?



States
Transitions

 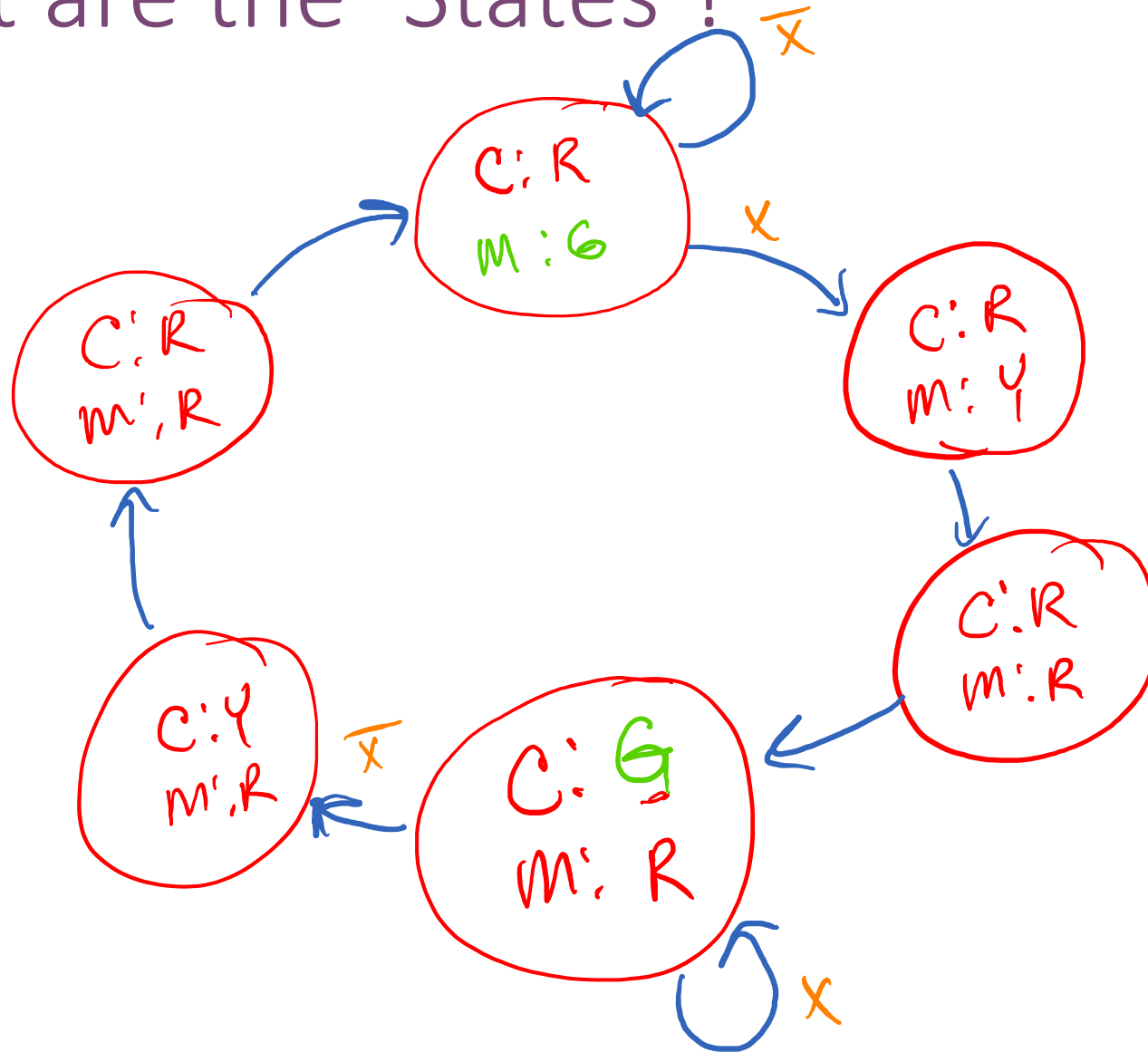

What are the 'States'?

  


What are the 'States'?

  



State	X	Next State
000	0	000
000	1	001
001	0	010
001	1	010
010	0	011
010	1	011
011	0	100
011	1	011
100	0	101
100	1	101
101	0	000
101	1	000

What are the 'States'?


 


State	X	Next State
✓ 0 0 0	0	000
✓ 0 0 0	1	001
✓ 0 0 1	0	010
✓ 0 0 1	1	010
✓ 0 1 0	0	011
✓ 0 1 0	1	011
✓ 0 1 1	0	100
✓ 0 1 1	1	011
✓ 1 0 0	0	101
✓ 1 0 0	1	101
1 0 1	0	000
1 0 1	1	000

What are the 'States'?

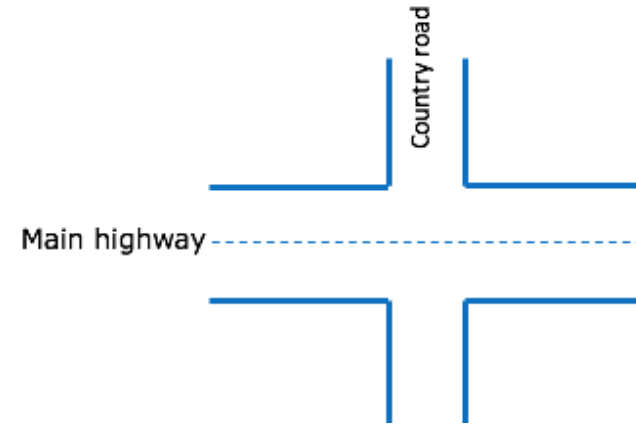 

What are the 'States'?

  

skip till next time

FSM: Simple Vending Machine

- You are designing a Vending Machine that dispenses Widgets for \$0.25/each.
- Your machine must accept any combination of nickels (N), dimes (D), and quarters (Q) to pay for the Widget.
- When the correct payment is secured, you dispense the Widget (`vend`), and reset the payment.
- If a customer overpays, you keep the extra money. 😊
 - Just to simplify things...

0¢
vend=0

magic



payed
vend=1

FSM: Vending Machine

Moore vs. Mealy Type FSMs


- Thus far we've done "Moore" Type
 - Moore Type: Outputs determined by the state (circle)
- Another technique: "Mealy" Type
 - Mealy Type: Output determined by the transition (arrow)
- Moore: Easier, but more states
- Mealy: Less states, more complicated transitions

Traffic Light: Moore vs. Mealy

  


Implementing FSMs with Circuits

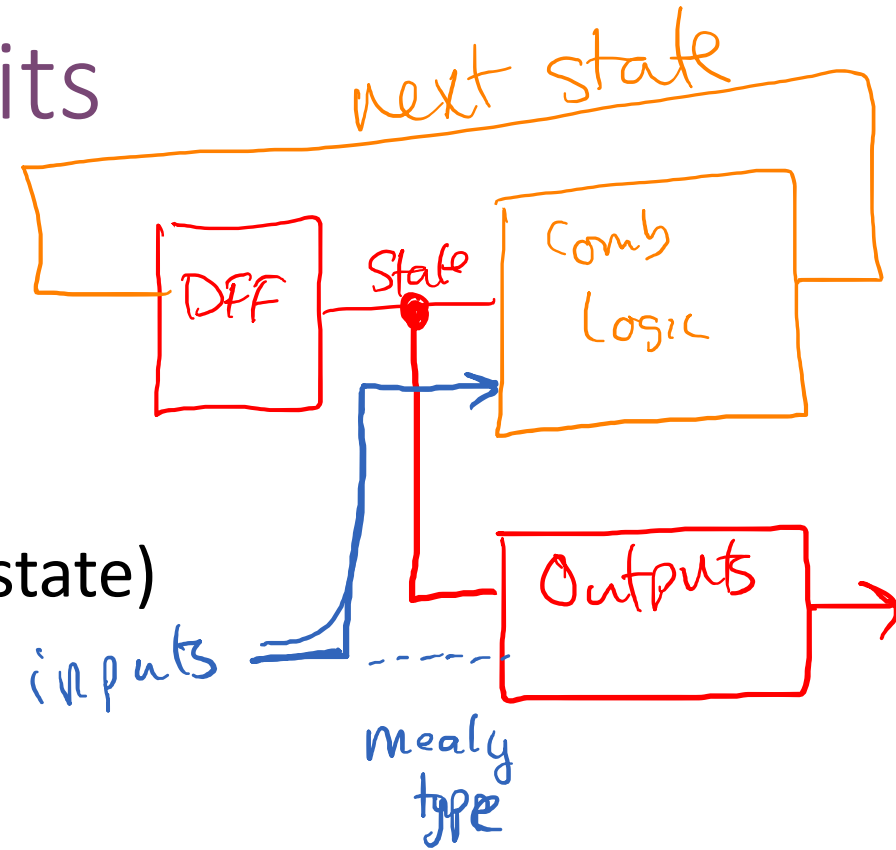- Encode each state as a number
 - Store this with DFF's
- Generate state transition logic (arrow to next state)
 - Use combinational logic
- Generate output given state + inputs
 - Use combinational logic



State Transition Encoding

 



State Machine Encoding

	<u>State</u>	<u>X</u>	<u>Next State</u>
0	00	0	00
1	00	1	01
2	01	0	10
3	01	1	10
4	10	0	11
5	10	1	10
6	11	0	00
7	11	1	00


Next State Logic

	State	X	Next State
0	00	0	00
1	00	1	01
2	01	0	10
3	01	1	10
4	10	0	11
5	10	1	10
6	11	0	00
7	11	1	00

NS_1 NS_0

  

Circuit Structure for FSMs


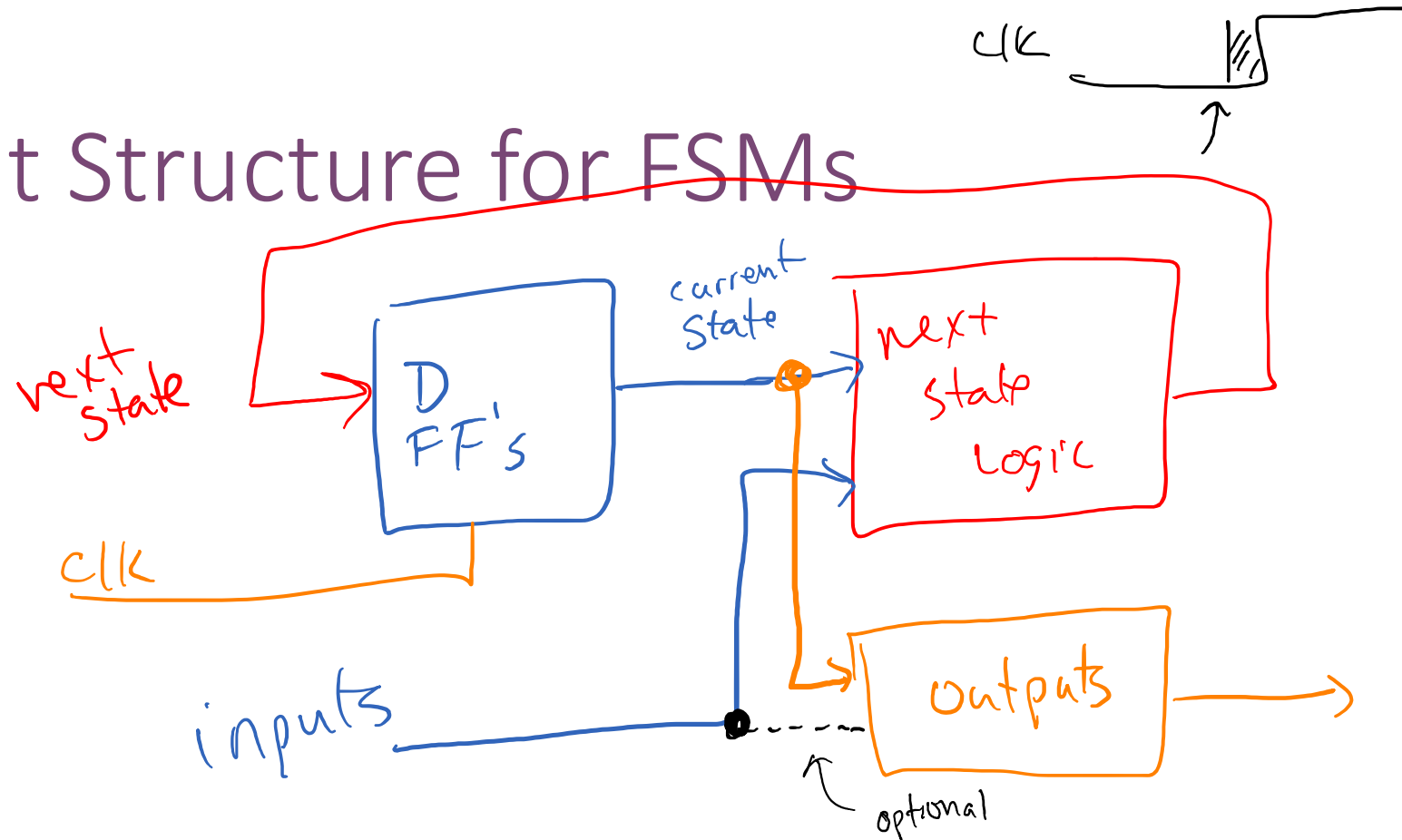


Moore Machine: outputs are a function of current state

Mealy Machine: outputs are a function of current state + inputs



Output Logic (Highway)

	<u>State</u>	<u>X</u>
0	00	0
1	00	1
2	01	0
3	01	1
4	10	0
5	10	1
6	11	0
7	11	1

 
 


Output Logic (Country Rd)

	State	X
0	00	0
1	00	1
2	01	0
3	01	1
4	10	0
5	10	1
6	11	0
7	11	1

  


State Machine to Logic

  


State Machine to Verilog

- Define states?

 

State Machine to Verilog


- Define states?

 

```
enum { ST_0, ST_1, ST_2, ST_3 } state, nextState;
```

State Machine to Verilog

- Build State Machine?

 


State Machine to Verilog

- Build State Machine?

```
always_ff @(posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end
```


- What is nextState?

 

State Machine to Verilog

```
always_ff @(posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end
```


- What is nextState?

 

State Machine to Verilog

```
always_ff @(posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end

 
always_comb begin
    nextState = state; //default
    case(state)
        ST_0: nextState = ST_1; //goto state 1
        ST_1: nextState = ST_2;
        ST_2: nextState = ST_3;
        ST_3: nextState = ST_0; //loop
        default: nextState = ST_0; //just in case
    endcase
end
```



State Machine to Verilog

- What is this missing?

 
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0: nextState = ST_1; //goto state 1
        ST_1: nextState = ST_2;
        ST_2: nextState = ST_3;
        ST_3: nextState = ST_0; //loop
        default: nextState = ST_0; //just in case
    endcase
end
```



State Machine to Verilog

- What is this missing?

 
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            nextState = ST_1;
        ST_1:
            nextState = ST_2;
        ST_2:
            nextState = ST_3;
        // ST_3 and default cases    endcase
    end
```



State Machine to Verilog

- What is this missing?
 
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            if (X) nextState = ST_1;
        ST_1:
            nextState = ST_2;
        ST_2:
            if (~X) nextState = ST_3;
        // ST_3 and default cases    endcase
    end
```




State Machine to Verilog

- What else is this missing?

```
always_comb begin
    nextState = state; //default


    case(state)
        ST_0:
            if (X) nextState = ST_1;

         // ST_1-3 and default cases
    endcase
end
```





State Machine to Verilog


```
always_comb begin
    nextState = state; //default
    Hryg = {0,0,1}; Cryg={1,0,0};
    case(state)
        ST_0: begin
            if (X) begin
                nextState = ST_1;
                Hryg = {0,1,0};
                Cryg = {1,0,0}; //optional
            end else begin
                nextState = ST_0; //optional
                Hryg = {0,0,1}; //optional
                Cryg = {1,0,0}; //optional
            end
        end
    end
    // ST_1-3 and default cases
endcase
end
```

 

State Machine in Logic

  

Circuit Structure for FSMs

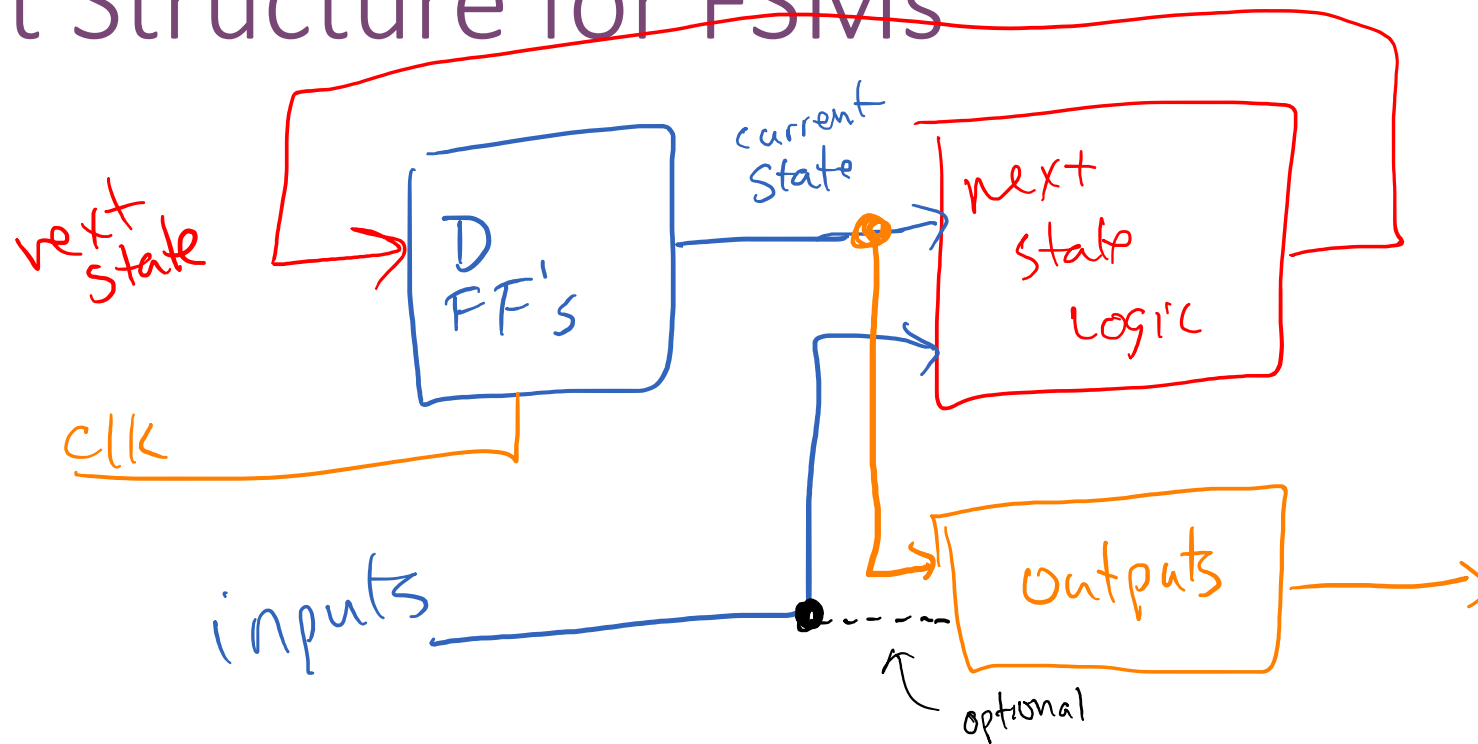

Moore Machine: outputs are a function of current state

Mealy Machine: outputs are a function of current state + inputs

Next Time

- More Finite State Machines (FSMs)